

NAME :- SANI KUMAR

BRANCH :- ECE

ROLL NO. :- 2001125



भारतीय सूचना प्रौद्योगिकी संस्थान भागलपुर

INDIAN INSTITUTE OF INFORMATION TECHNOLOGY BHAGALPUR

(An Institute of National Importance under Act of Parliament)

VLSI LAB MANUAL REPORT

NAME :- SANI KUMAR

ROLL NO. – 2001125


DEP. – ECE

SUMMITTED TO:- RAJAN SIR

EXPERIMENT -6

AIM :- Half Adder using NAND Gate

 THEORY:- Half adder is a combinational circuit that performs the simple addition of two single-bit binary numbers and produces a 2-bit number. The LSB of the result is the Sum (usually represented as Sum or S_0 or Σ_0) and the MSB is the Carry (usually represented as C_{OUT}).





TRUTH TABLE-

INPUT		OUTPUT	
A	B	Sum	
0	0	0	
0	1	1	
1	0	1	
1	1	0	

PROCEDURE

1. Draw the schematic of the HALF ADDER using the NAND gate.
2. Perform Transient Analysis of the HALF ADDER circuit.
3. Obtain the output waveform from W-edit.
4. Obtain the spice code using T-edit.

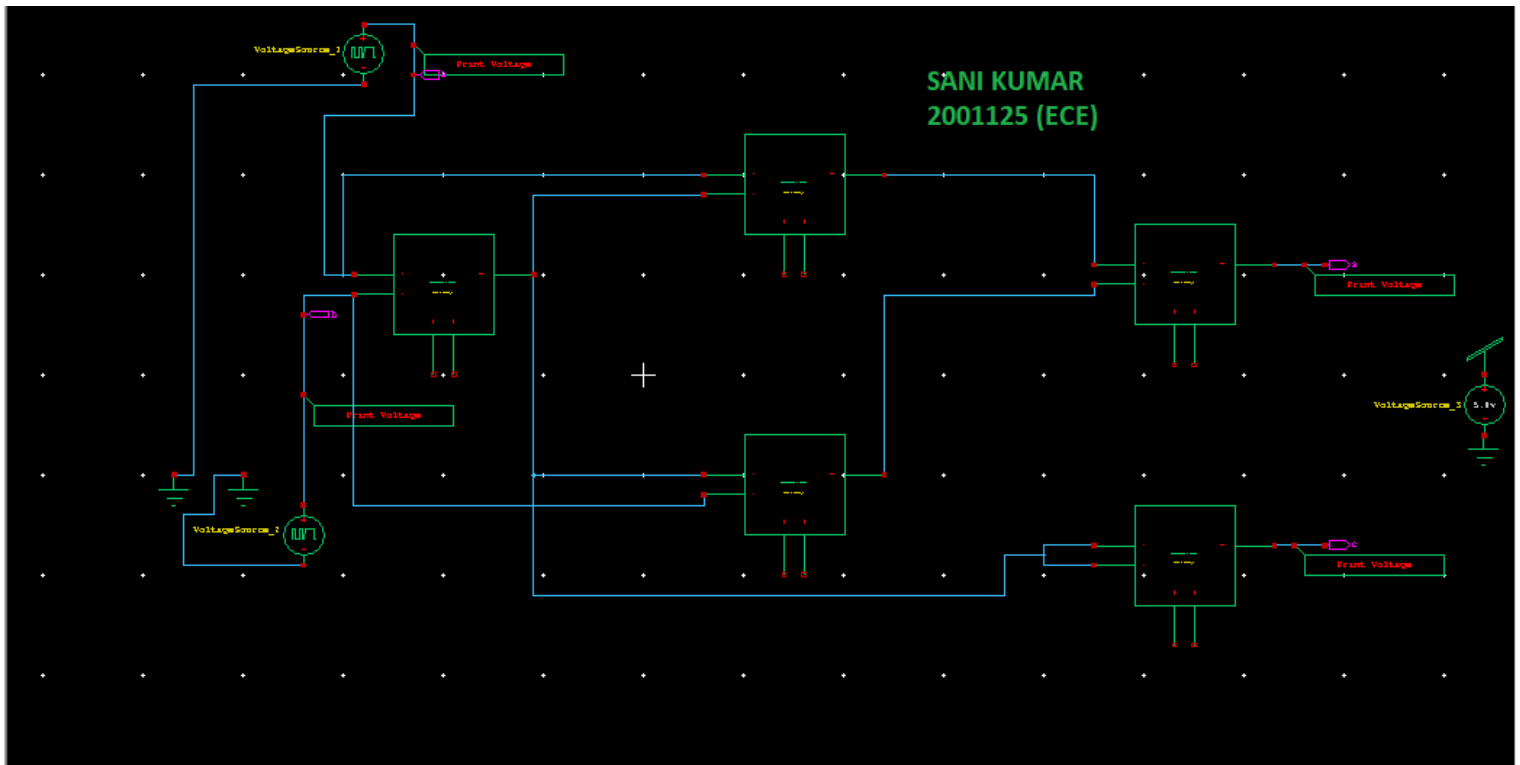Circuit diagram-**OUTPUT-**

 **AIM**


. Full Adder using NAND Gate

APPARATUS REQUIRED:

NAND GATE(COMPLEX CMOS CIRCUIT), BIT VOLTAGE, GROUND, VDD

THEORY:


Full adder is a digital circuit used to calculate the sum of three binary bits, which is the main difference between this and half adder. Two of the three bits are same as before which are A, the augend bit and B, the addend bit. The additional third bit is carry bit from the previous stage and is called Carry-in, generally represented by C_{IN} . It calculates the sum of three bits along including the carry. The output carry is called Carry-out and is represented by C_{OUT} .

 


TRUTH TABLE-

Inputs			Outputs	
A	B	C _{in}	C _{out} (Carry)	S (Sum)
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Circuit diagram-

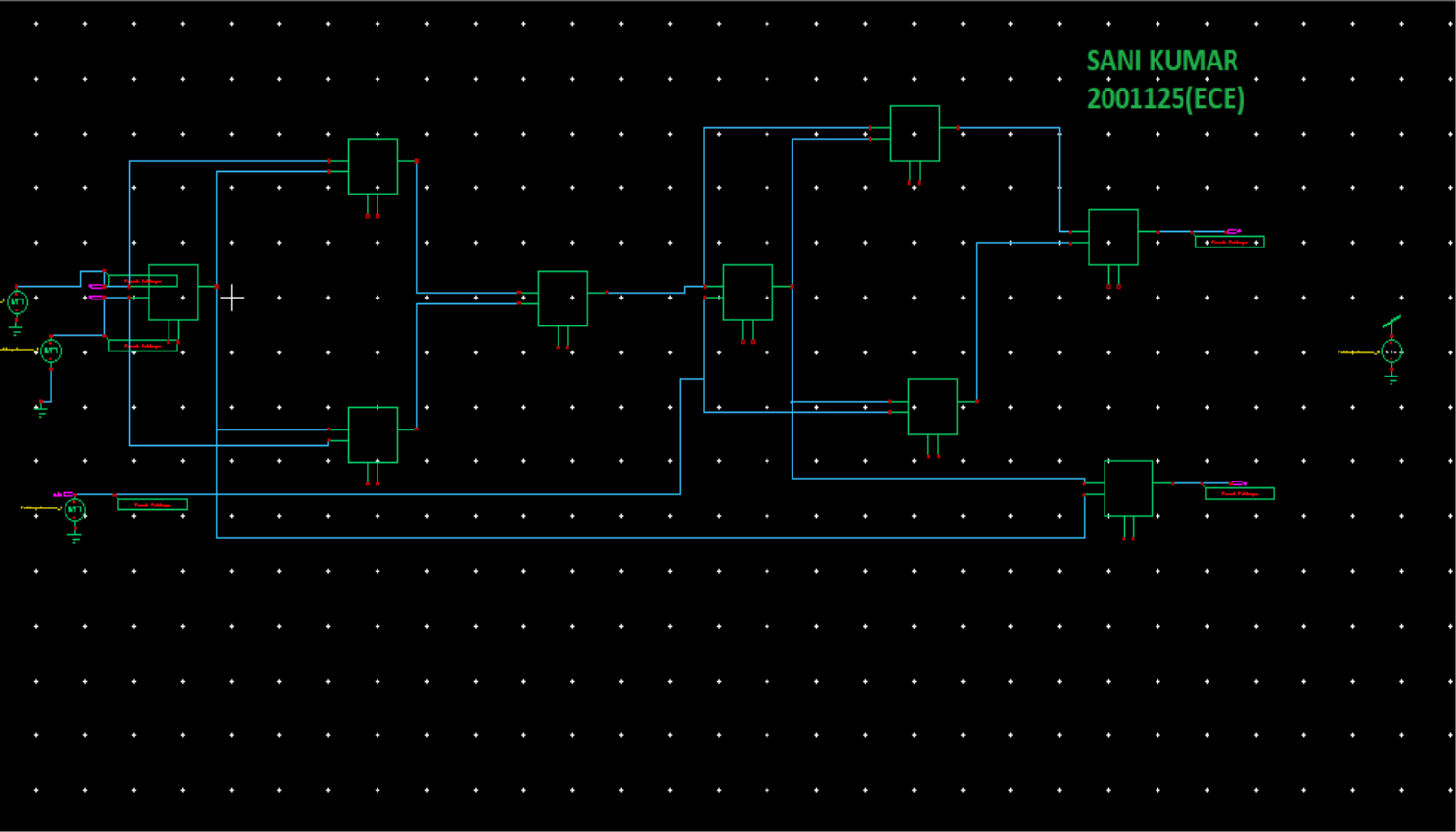

Output-

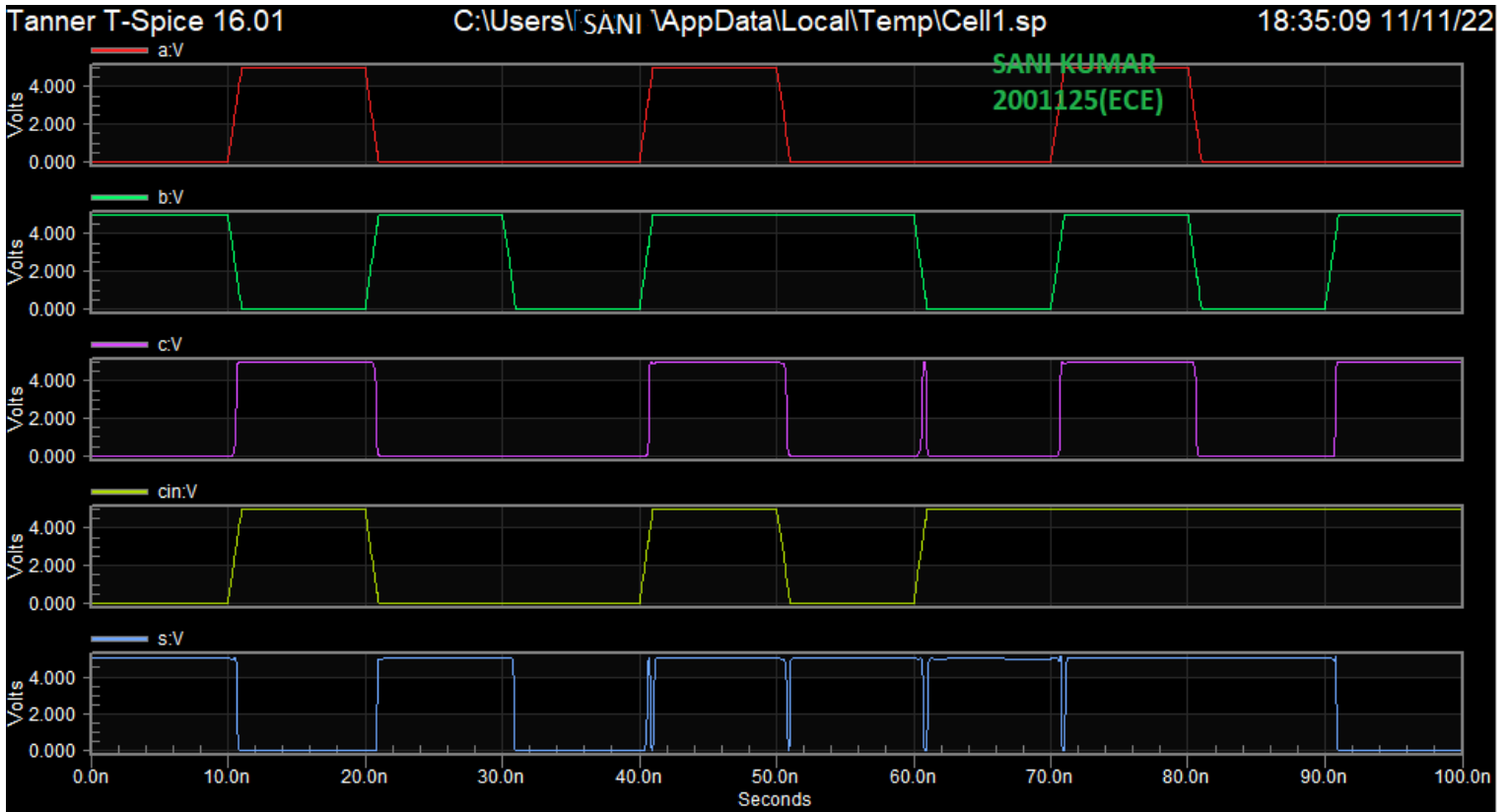

EXPERIMENT 7

AIM

4:1 Multiplexer using NAND Gate

APPARATUS REQUIRED:

NAND GATE(COMPLEX CMOS CIRCUIT), BIT VOLTAGE, GROUND, VDD,

THEORY:

Building 4x1 mux directly from NAND gates: The logical equation of a 4x1 multiplexer is given as:

$$Y = (S1' S0' A + S1' S0 B + S1 S0' C + S1 S0 D)$$

where S_1 and S_0 are the selects of the multiplexer and A, B, C and D are the multiplexer inputs.

Now, using De-morgan's law ($m + n = (m'n')'$)

The above equation turns into,

$$Y = ((S_1' S_0' A)' (S_1' S_0 B)' (S_1 S_0' C)' (S_1 S_0 D)')'$$

In other words,

$$Y = \text{NAND} (\text{NAND}(S_1', S_0', A), \text{NAND}(S_1', S_0, B), \text{NAND}(S_1, S_0', C), \text{NAND}(S_1, S_0, D))$$

S_0	S_1	Output
0	0	A
0	1	B
1	0	C
1	1	D



 


Fig. 1: 4x1 Multiplexer

Circuit diagram-

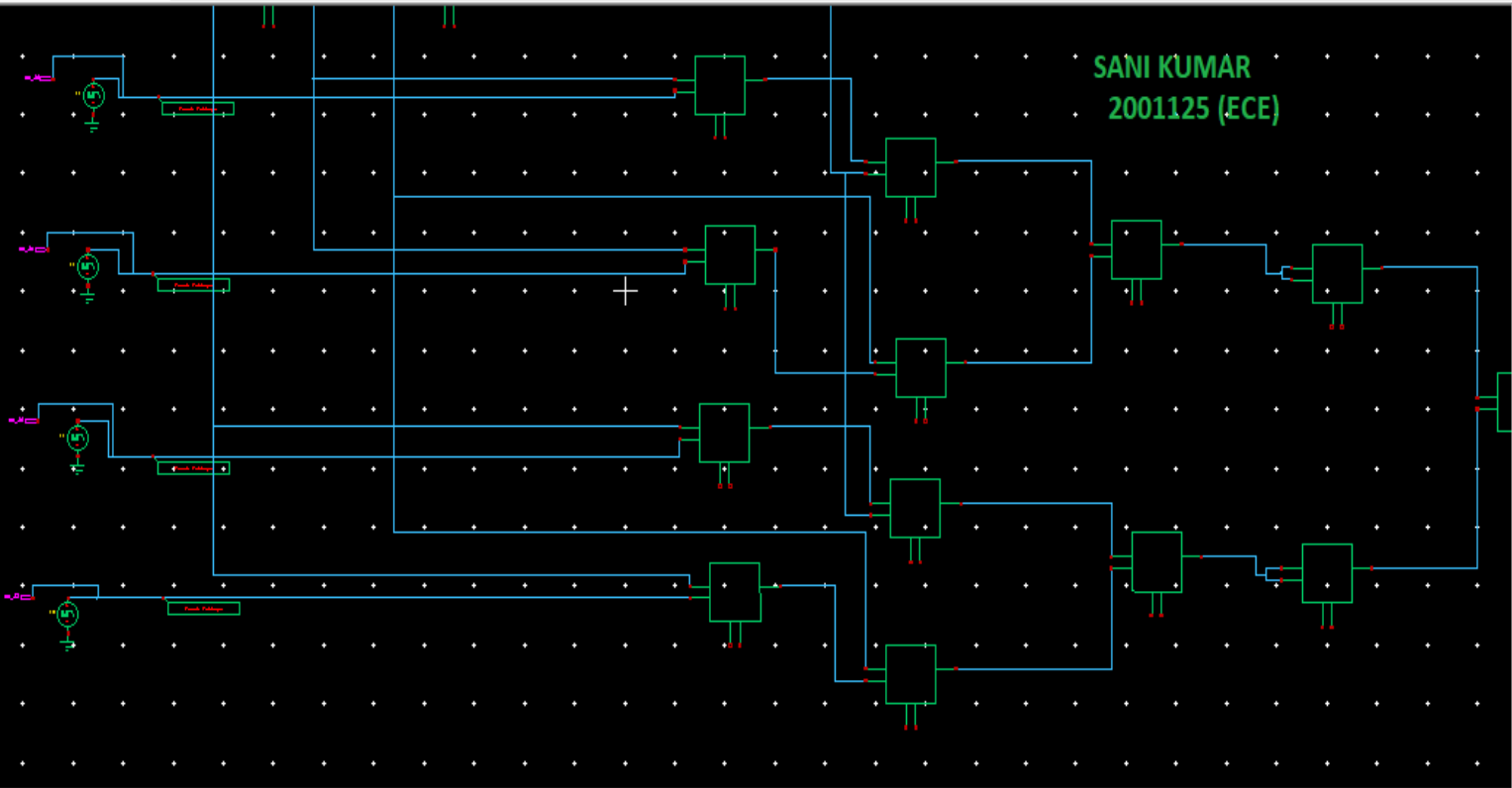

Output-

 

EXPERIMENT 8

AIM

DC and transient analysis of dynamic logic circuit.


APPARATUS REQUIRED:

PMOS, NMOS, VDD, GROUND, OUTPUT INPUT PORT


THEORY:

Dynamic circuit class, which relies on temporary storage of signal values on the capacitance of high impedance circuit nodes. In this section, an alternate logic style called dynamic logic is presented that obtains a similar result, while avoiding static power consumption. With the addition of a clock input, it uses a sequence of precharge and conditional evaluation phases. The basic construction of an (n-

 type) dynamic logic gate is shown in Figure. The PDN (pull-down network) is constructed exactly as in complementary CMOS. The operation of this circuit is divided into two major phases: precharge and evaluation, with the mode of operation determined by the clock signal CLK.





(a) n-type network

 


(b) Example


Circuit diagram- DC ANALYSIS

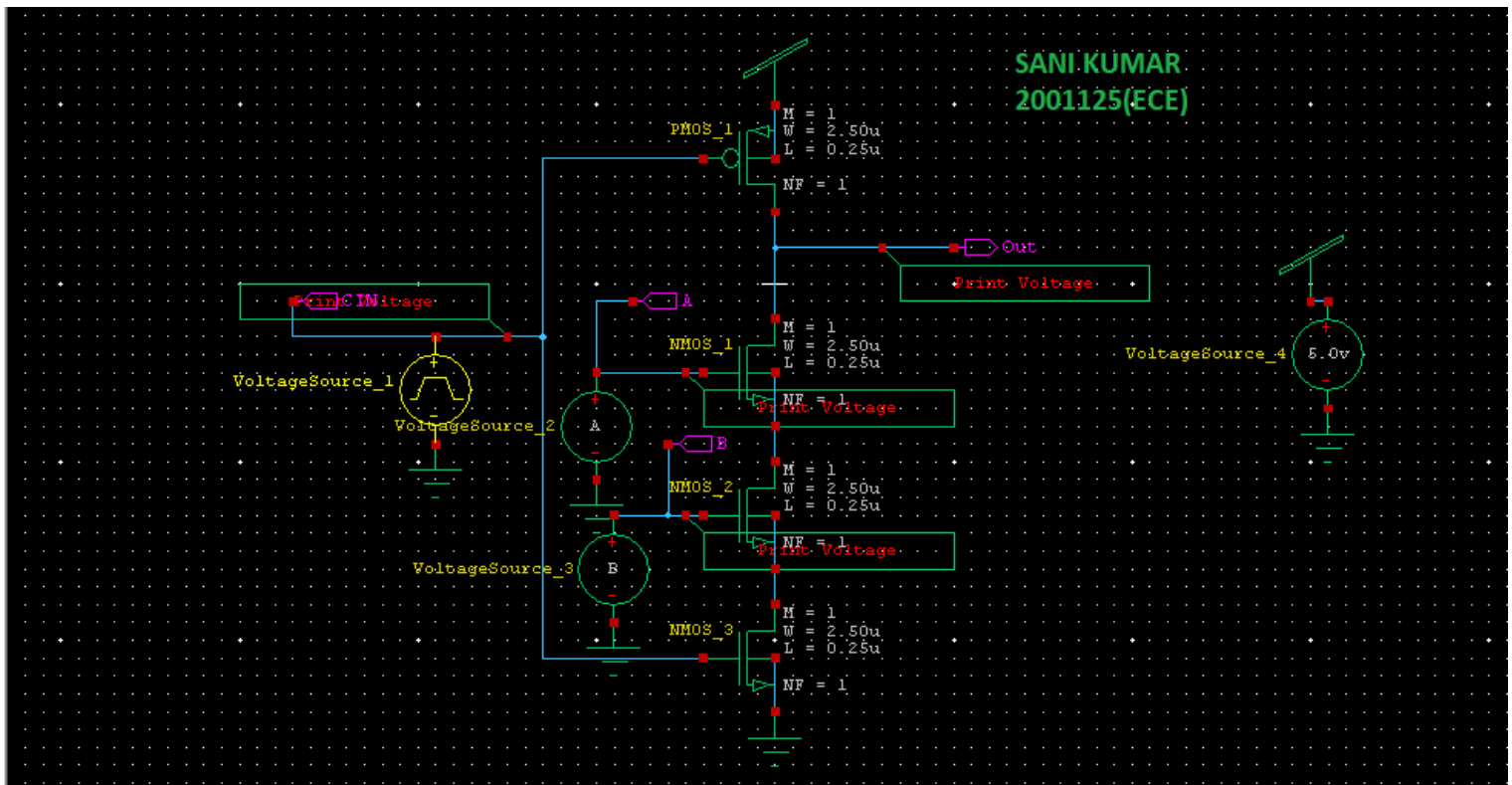

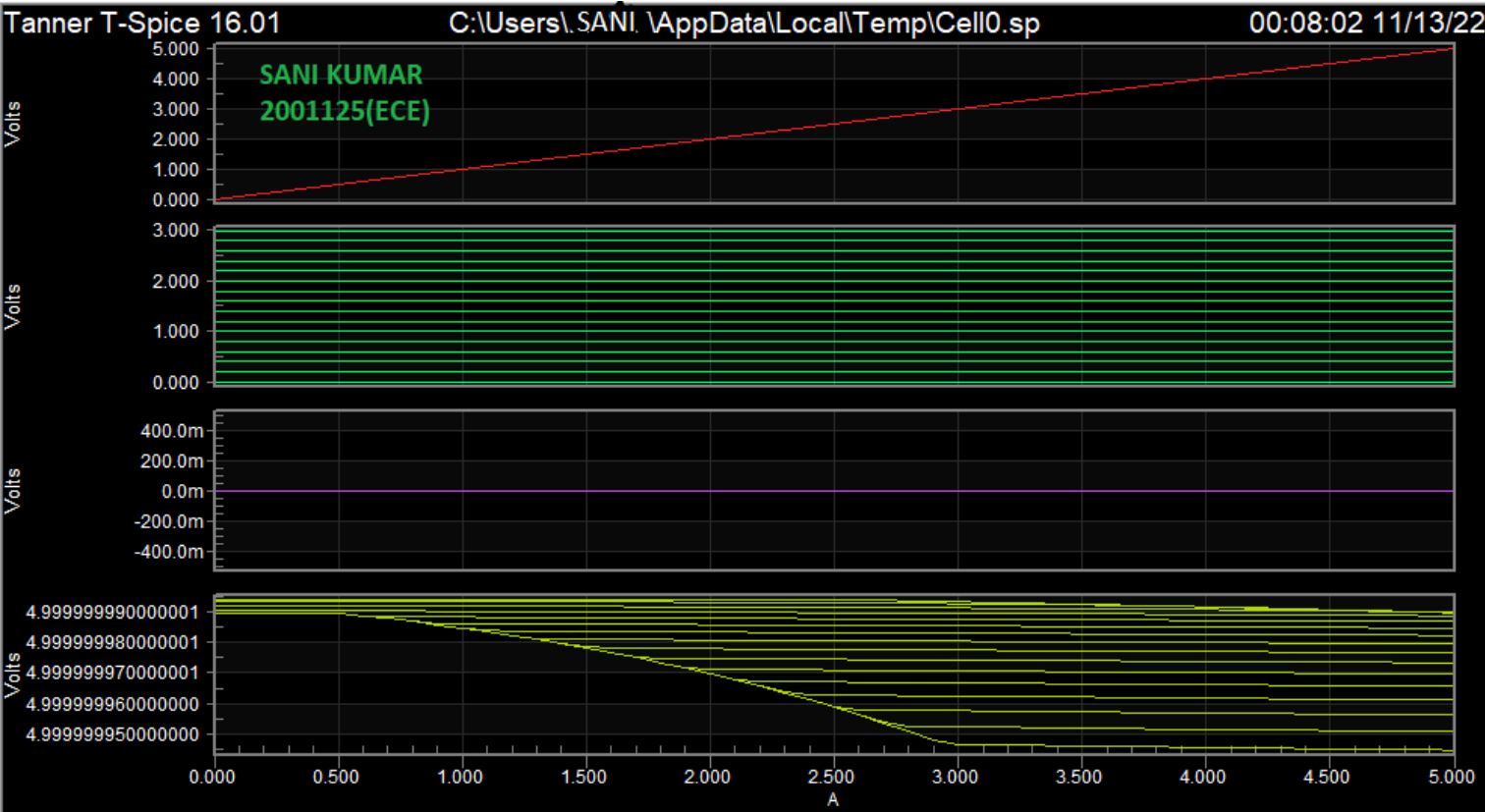

TRANSIENT ANALYSIS-

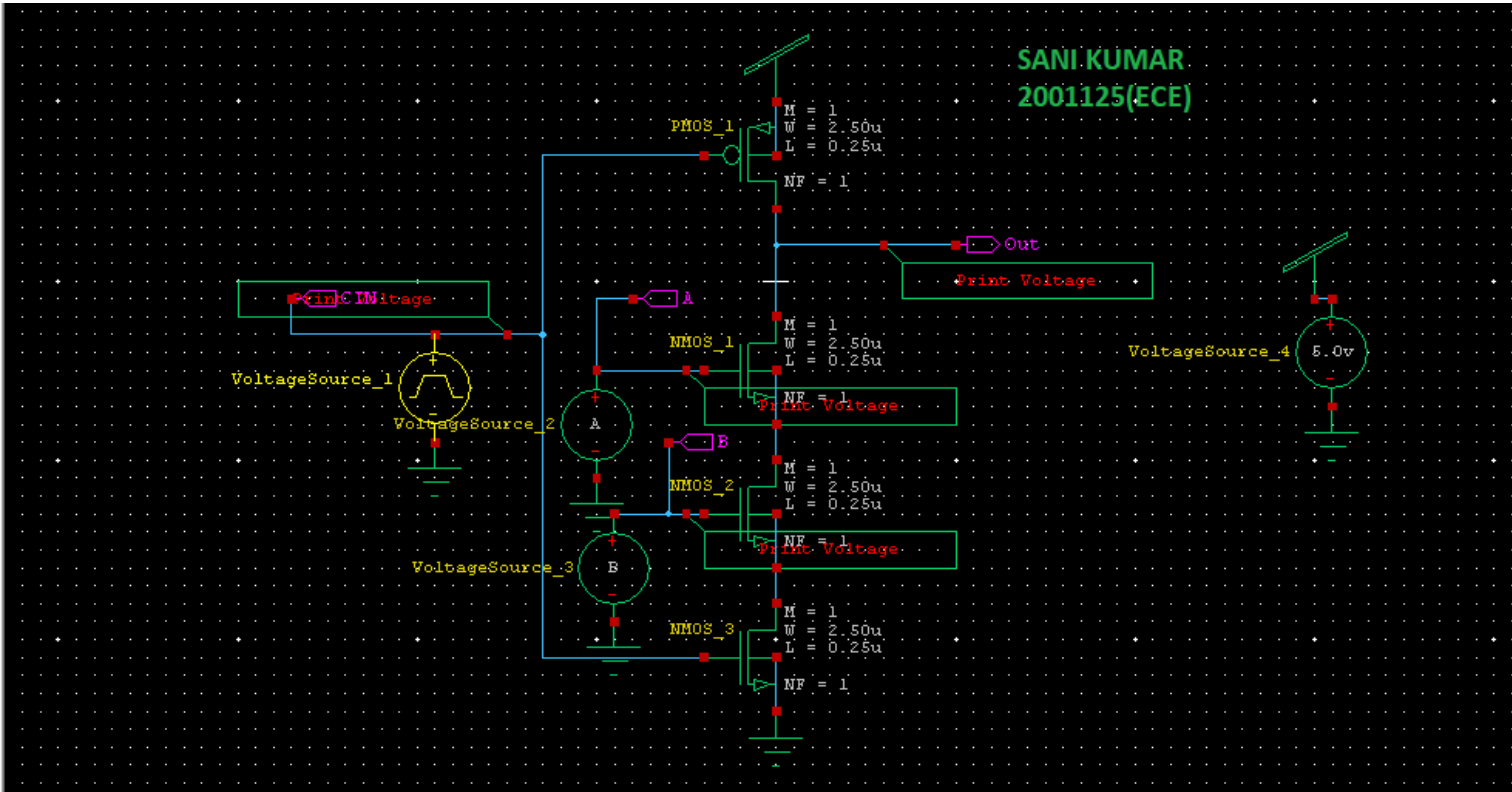

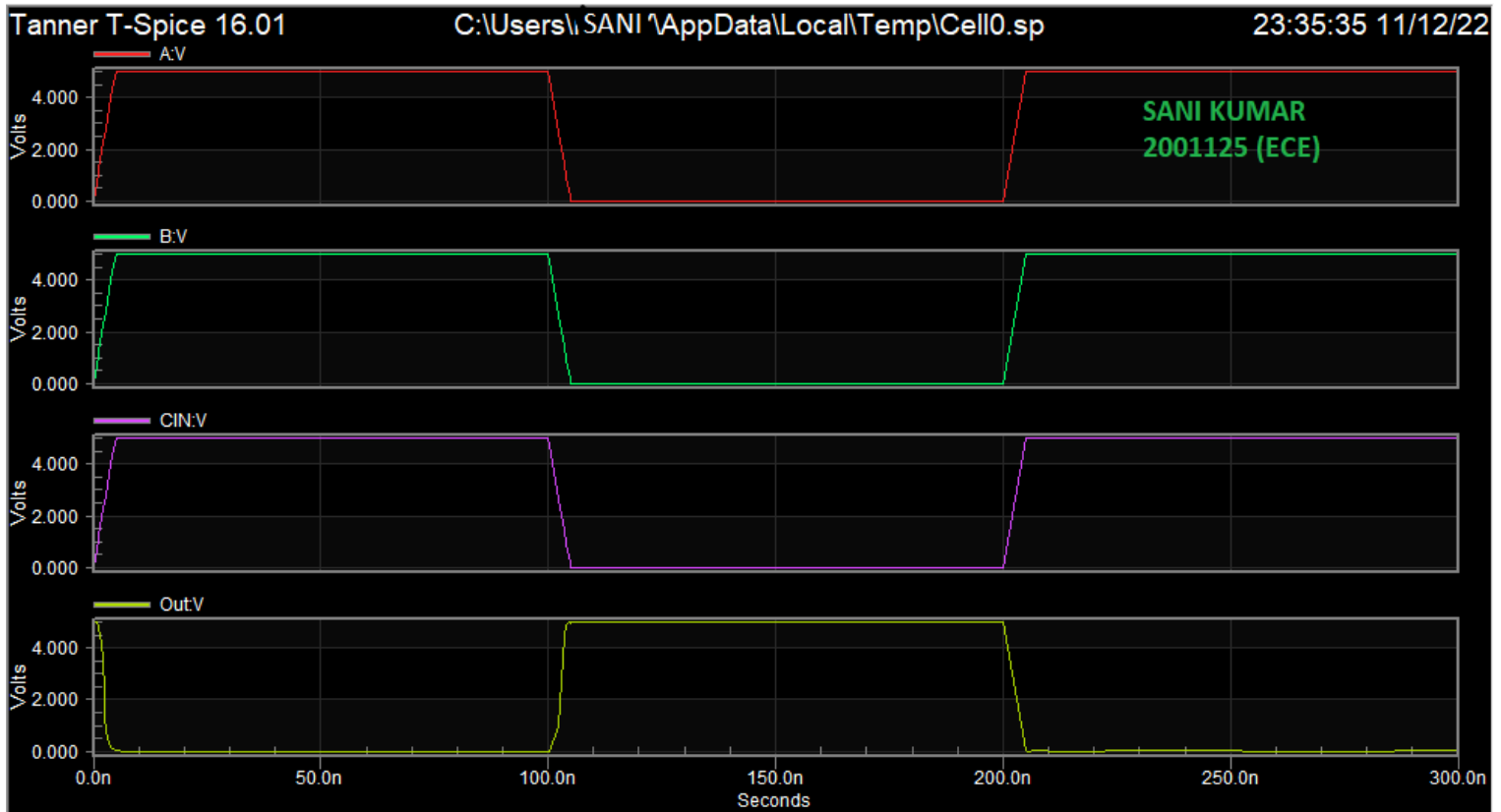

AIM


DC and transient analysis of RATIOED logic circuit.

APPARATUS REQUIRED:


PMOS, NMOS, VDD, GROUND, OUTPUT INPUT PORT

THEORY:

 Ratioed circuits use weak pull-up devices and stronger pull-down devices. They reduce the input capacitance and hence improve logical effort by eliminating large pMOS transistors loading the inputs but depend on the correct ratio of pull-up to pull-down strength.





A	B	V_o
0	0	1
0	1	1
1	0	1
1	1	0

 



DC ANALYSIS-

CIRCUIT DIAGRAM –

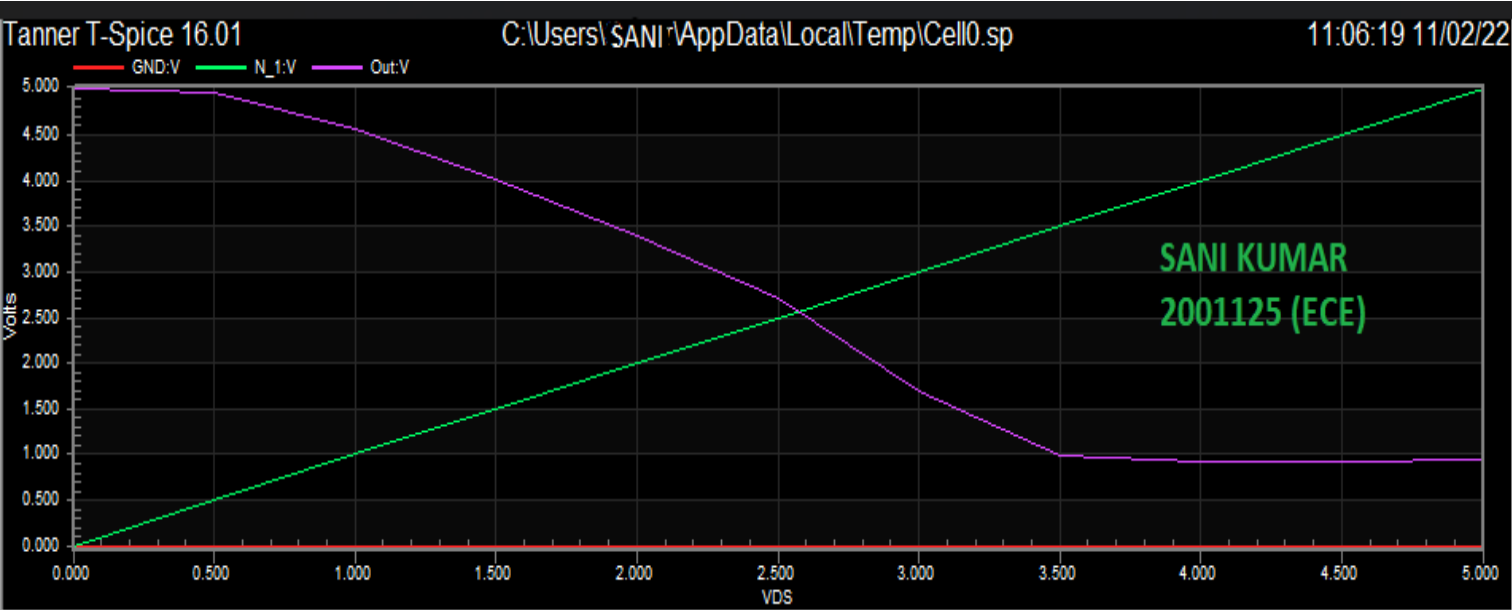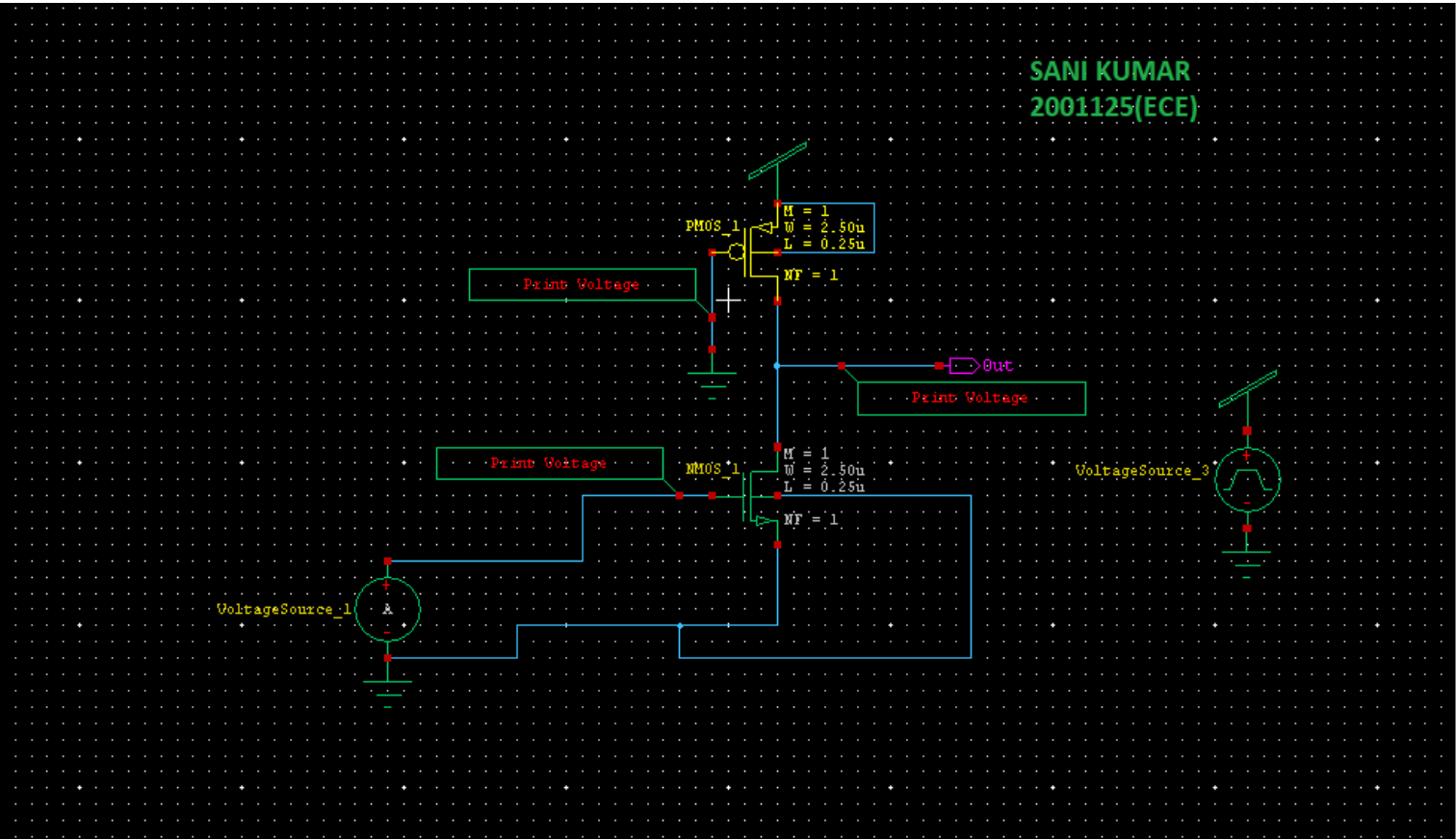

TRANSIENT ANALYSIS-

Circuit diagram-

 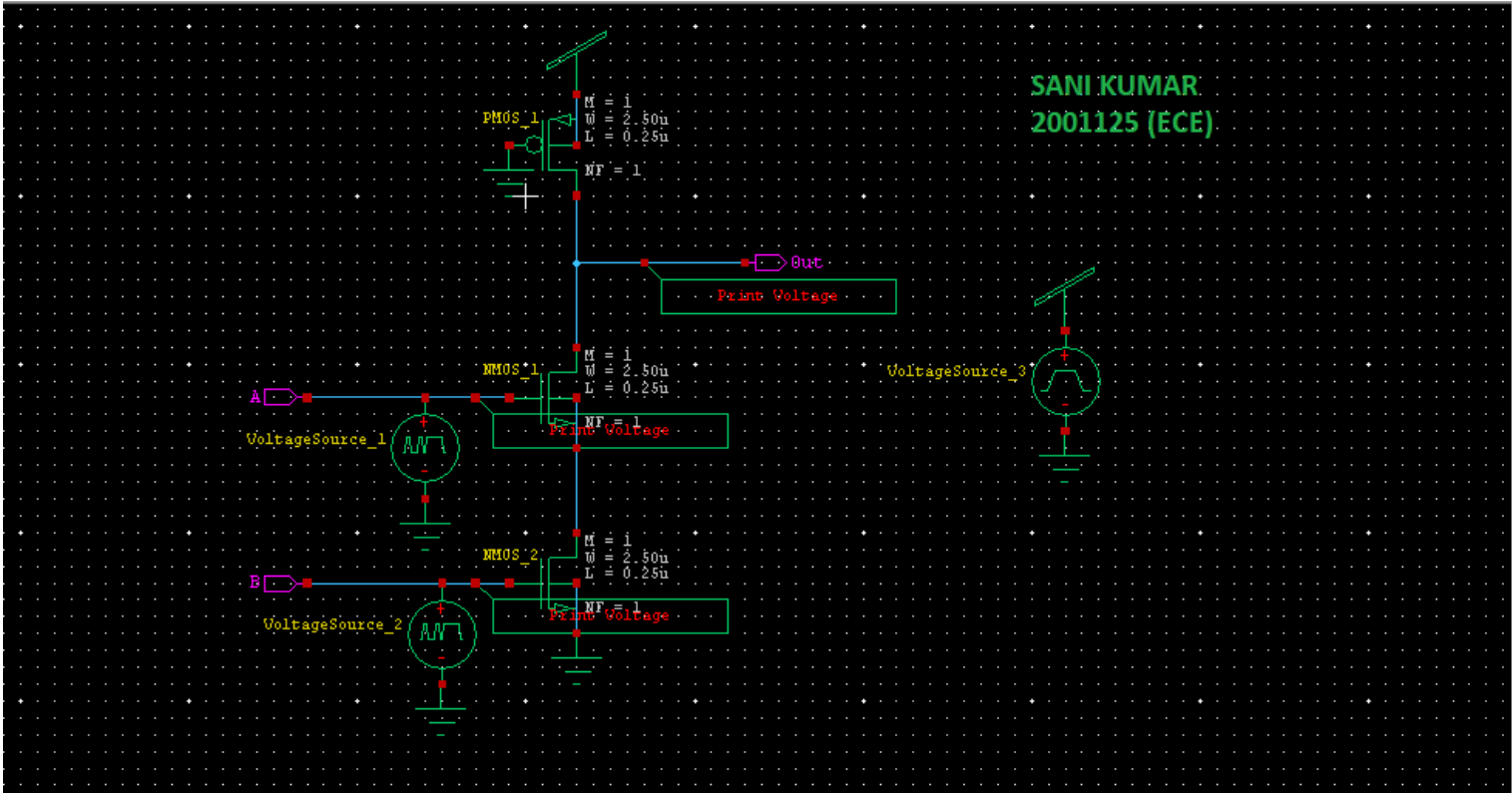

EXPERIMENT 9**AIM**

DC and transient analysis of RATIOED logic circuit.

APPARATUS REQUIRED:

PMOS, NMOS, VDD, GROUND, OUTPUT INPUT PORT

THEORY:

A transmission gate is an electronic element and good non mechanical relay built with CMOS technology. It is made by parallel combination of nMOS and pMOS transistors with the input at the gate of one transistor (C) being complementary to the input at the gate () of the other.



 
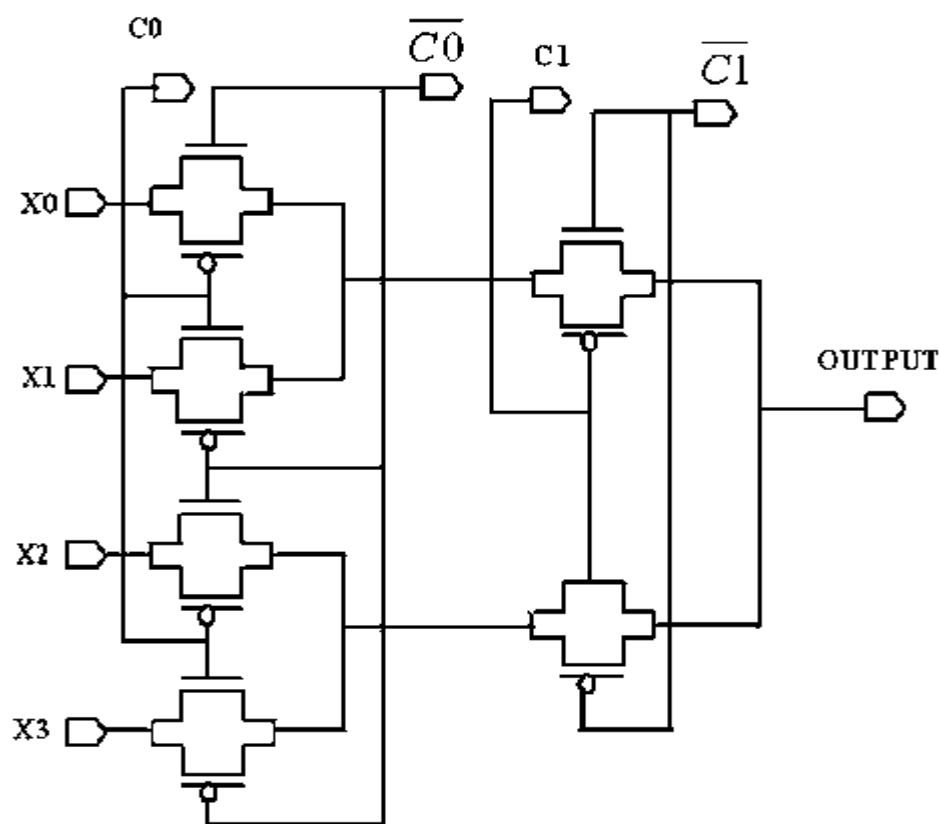


Fig.4: Symbol for transmission gate

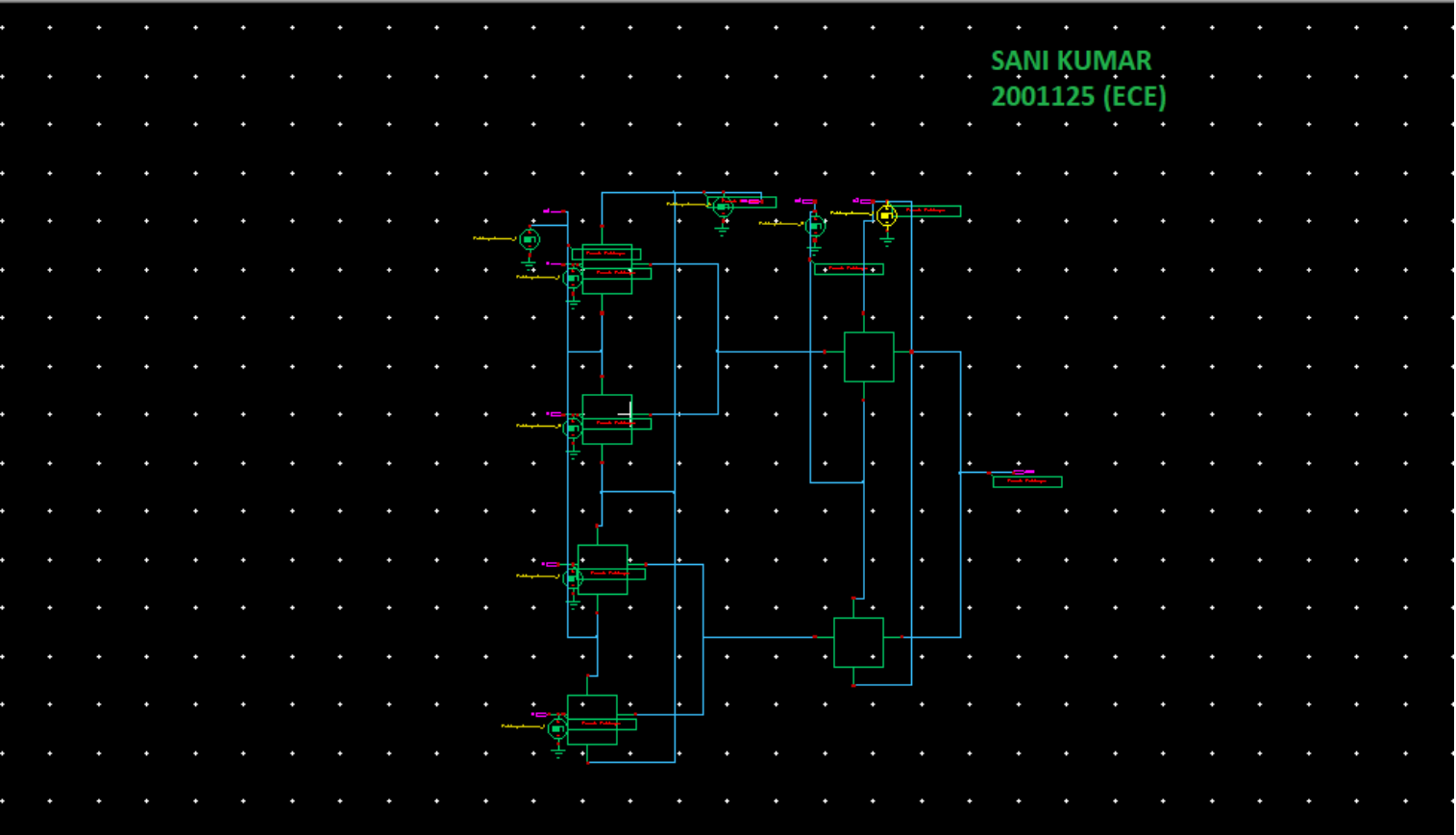

Transmission gate construction –

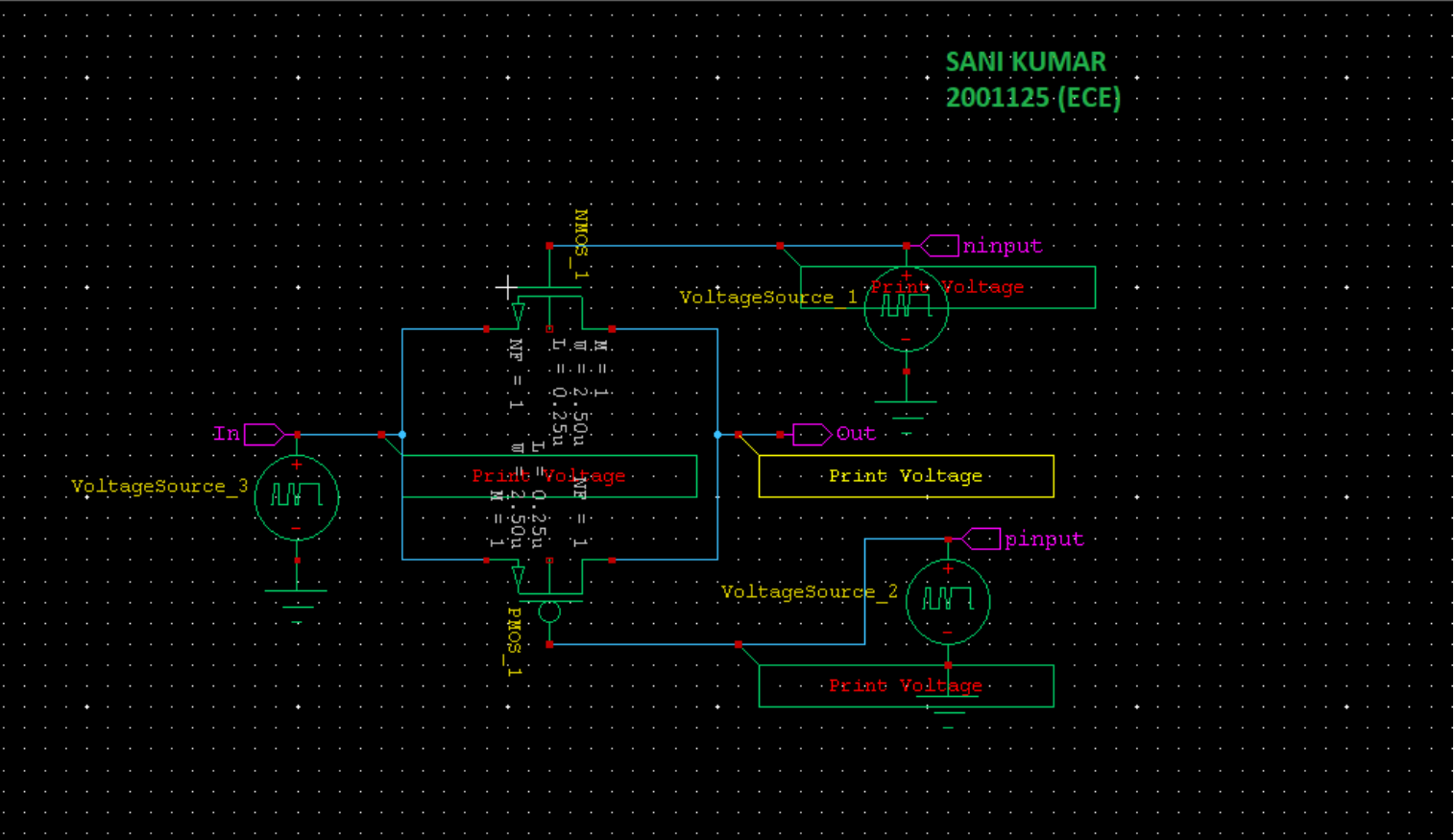

OUTPUT :-

